
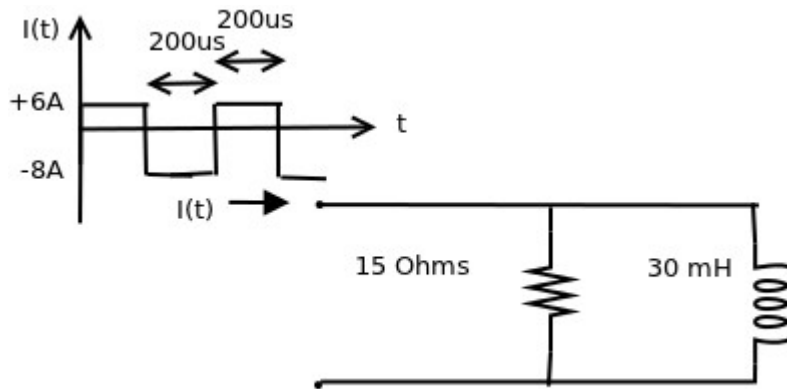


**Phys 2201 Electricity and Magnetism**  
**Homework #18 – Due Mar. 22, 2016 by 3pm**  
**(hand in to drop box outside 3L24)**

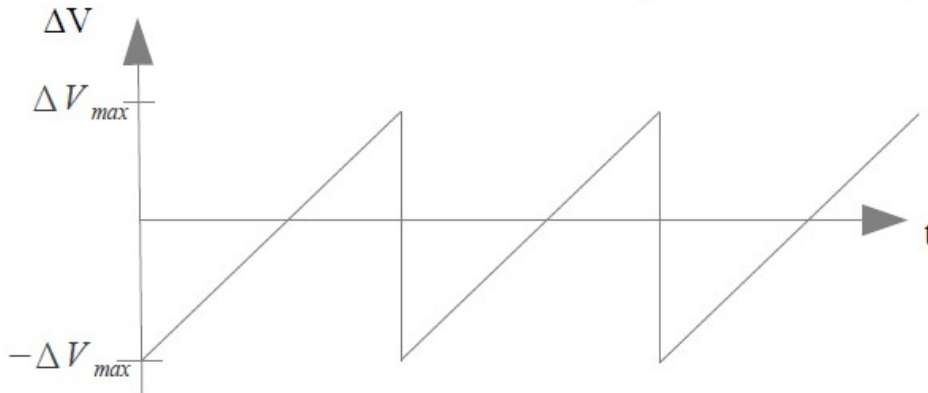
1. An current square wave with period 400  $\mu\text{s}$ , that goes to +6 A and down to -8 A is applied to the circuit below. What is the Emf across the inductor as a function of time for the first upswing and downswing? Plot or sketch the curve, and derive  $\text{Emf}(t)$  for the first upswing and downswing of the current. Assume that the initial current in the inductor is -1.35 A.



2. Show that the RMS value of the saw-tooth voltage shown in the figure below is  $\Delta V_{max}/\sqrt{3}$ .



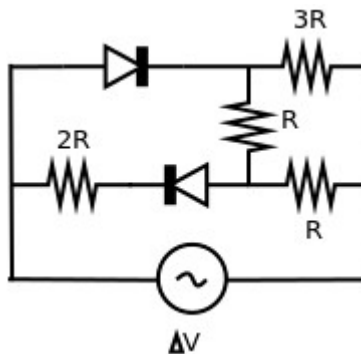3. Find the average power delivered by the power supply in terms of the AC voltage amplitude  $\Delta V$  and  $R$  for the circuit below.



4. A  $6.5 \mu\text{F}$  capacitor is charged by a  $24 \text{ V}$  DC power supply. The fully charged capacitor is then discharged through a  $2 \text{ mH}$  inductor. Find the maximum current in the resulting oscillations.

5. In the RLC circuit below, the switch has been in position 'a' for a long time. (a) Find an expression for the charge as a function of time on the capacitor when the switch is flipped to position 'b', when  $R=18 \text{ Ohms}$ ,  $L=5.8 \text{ mH}$ , and  $C=2.20 \mu\text{F}$ , and  $V=8.0 \text{ V}$ . (b) Plot or sketch the charge versus time. (c) What value of  $R$  should be chosen to give critical-damping?

