

PHYS-2201 Electricity and Magnetism

Assignment 11

Due: Tuesday, Jan. 19, 2015, by 3pm (at dropbox outside 3L24)

1. (5 points) Three equal resistors (R) are connected to a power supply as shown in the left circuit of FIG. 1. When the switch S is opened after having been closed for a long time, what happens to:
 - (a) the voltage drop across each resistor,
 - (b) the current flow through each resistor, and
 - (c) the terminal voltage of the battery?
 - (d) If the emf of the battery is 9.0 V , what is the terminal voltage when the switch is closed if the internal resistance is $2.50\ \Omega$ and $R = 12.5\ \Omega$?
 - (e) Using the same numbers, what is the terminal voltage after the switch is opened again?

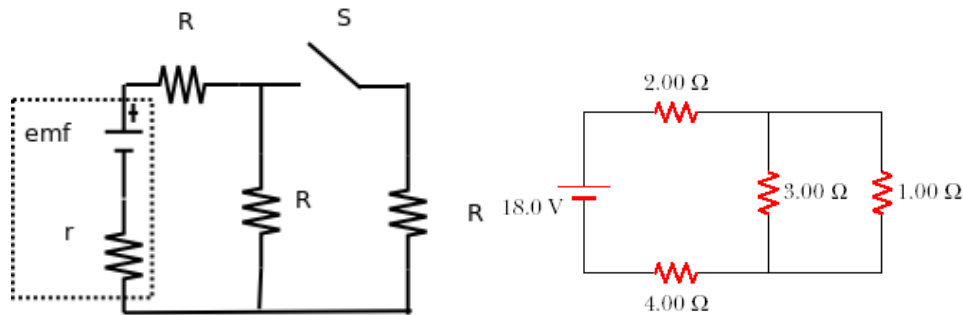


Figure 1: Problem 1 (left), and problem 2 (right).

2. (5 points) Calculate the power delivered to each resistor of the circuit on the right in FIG. 1.
3. (5 points) Solve for the currents in each of the resistors in FIG. 2 by hand. Use $R_1 = 5\ \Omega$, $R_2 = 15\ \Omega$, $R_3 = 5\ \Omega$, $R_4 = 8\ \Omega$, $R_5 = 3\ \Omega$, $R_6 = 2\ \Omega$, $V_1 = 3\text{ V}$, $V_2 = 6\text{ V}$, and $V_3 = 9\text{ V}$.
4. (5 points) The switch S has been closed for a long time, and the electric current shown in FIG. 3 carries a constant current. The values of the components in the circuit are $C_1 = 2.10\ \mu\text{F}$, $C_2 = 3.50\ \mu\text{F}$, $R_1 = 2.80\ \text{k}\Omega$, and $R_2 = 1.70\ \text{k}\Omega$. The power delivered to R_2 is 2.5 W .
 - (a) Find the charge on C_1 .
 - (b) Now the switch is opened. After 1.5 ms , by how much has the charge on C_2 changed?

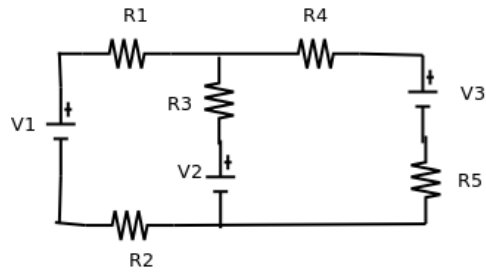


Figure 2: Problem 3.

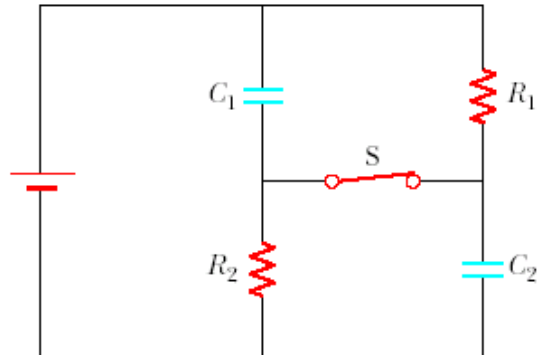


Figure 3: Problem 4.

5. (5 points) Determine the current through the switch as a function of time when the switch in the circuit in FIG. 4 is closed, after having been open for a long time. Write down the current in terms of V_{in} , R_1 , R_2 , and C , then plug in the values. How much energy is stored in the capacitor when it is fully charged?

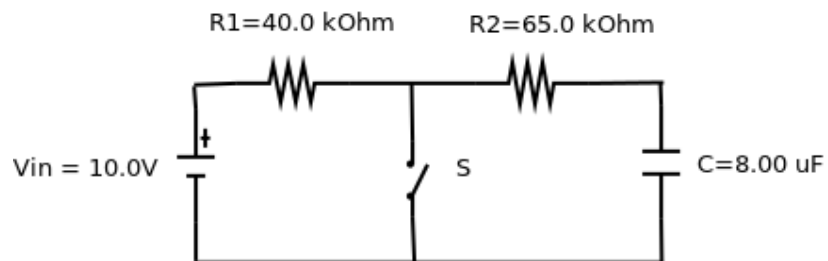


Figure 4: Problem 5.